

Aaron Hong (ahong02)
Stephen Macris (smacris)
EE 469
9 May 2023

Lab 3 Report

Procedure

In this lab, the single cycle processor was upgraded to a pipelined processor. Stalling, flushing, and forwarding logic were added to handle data and control hazards.

Results

1110000001001111000000000000001111	// 0	MAIN	SUB	R0	R15	R15	R0 = 0
111000101000000000001000000000001	// 4		ADD	R1	R0	#1	R1 = 1
1110000110000000000010000000000001	// 8		ORR	R2	R0	R1	R2 = 1
1110001010000000000010000000000010	// 12		ADD	R2	R0	#2	R2 = 2
1110001001010010000000000000000000	// 16		SUBS	R0	R2	#0	R0 = 2
0000101000000000000000000000000001	// 20		BEQ		TAG1		
1110000000000000100010000000000000	// 24		AND	R2	R2	R0	R2 = 2
1110000000000000100001000000000000	// 28		AND	R1	R2	R0	R1 = 2
1110000010000000110010000000000000	// 32	TAG1	ADD	R9	R1	R0	R9 = 4
111001011000000010010000000001001	// 36		STR	R9	[R0, #9]		
111001011001000000110000000001001	// 40		LDR	R3	[R0, #9]		R3 = 4
1110000000000000110010000000000010	// 44		AND	R2	R3	R2	R2 = 0

Figure 1: Test assembly instructions with expected register outputs

 


Figure 2: Simulation waveform

As shown in Figure 1 and 2, the pipelined processor is executing the instructions correctly. Stalling, flushing, and forwarding processes are also demonstrated. Figure 2 will be investigated more thoroughly in the following sections. Figures 3, 4, and 5 are magnified portions of Figure 2.

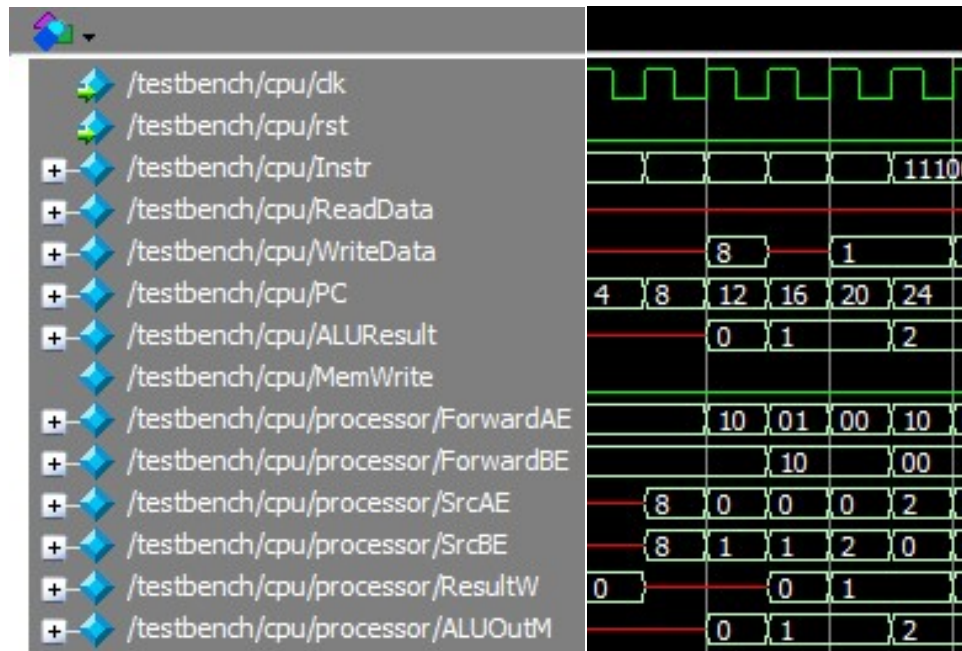


Figure 3: Forwarding signals

When PC=12, instruction 4 is in the execution stage and instruction 0 is in the memory stage. Since source register A of instruction 4 is the same as the destination register of instruction 0, there is a match between execute and memory stages and ForwardAE is set to 10. Hence, the data from the memory stage is forwarded to the execution stage: SrcAE = ALUOutM.

When PC=16, instruction 8 is in the execution stage and instruction 0 is in the writeback stage. Since source register A of instruction 8 is the same as the destination register of instruction 0, there is a match between execute and writeback stages and ForwardAE is set to 01. Hence, the data from the writeback stage is forwarded to the execution stage: SrcAE = ResultW.

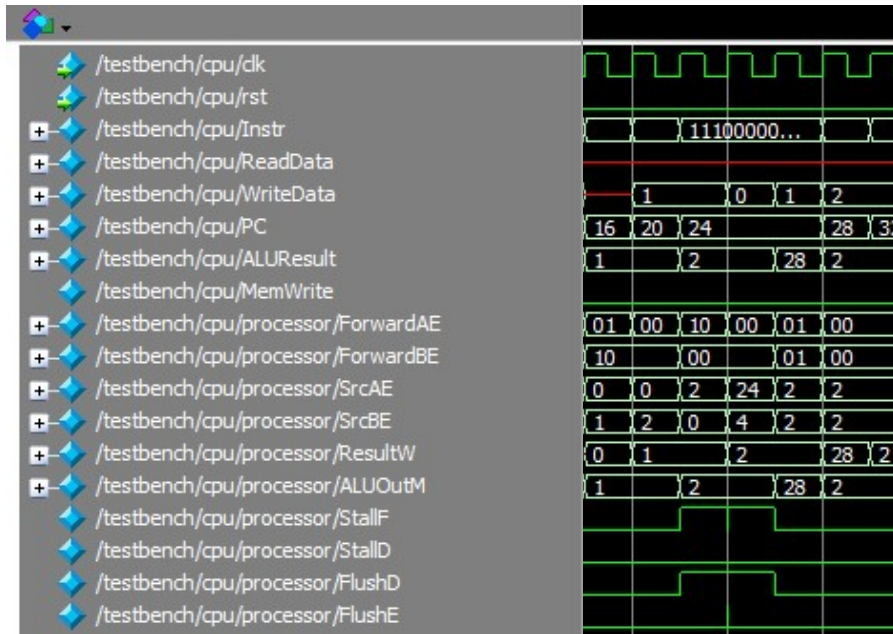


Figure 4: Branch flushing

Figure 4 shows that the two cycles of instruction are being flushed when the branch instruction (instruction 20) enters the decode stage.

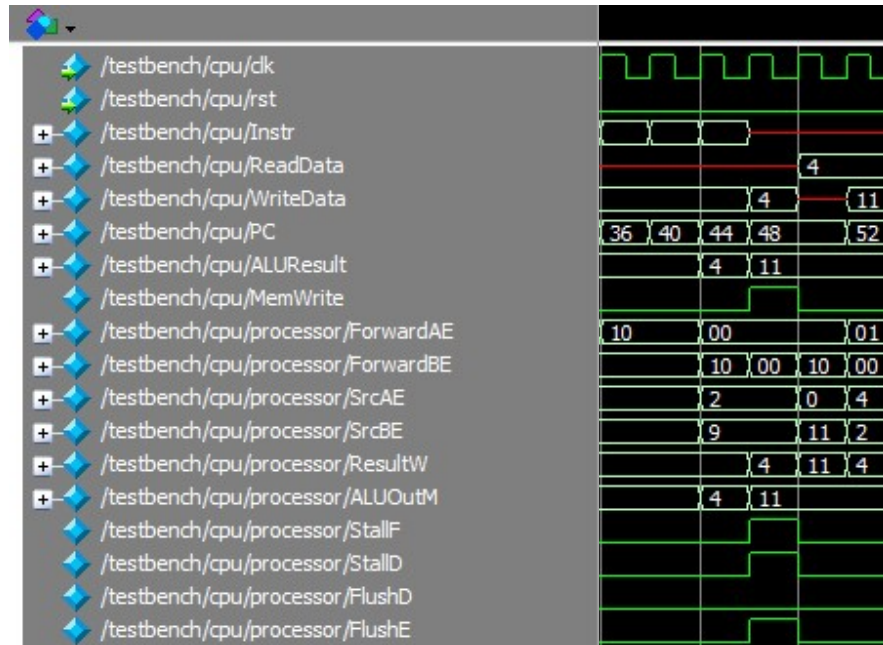


Figure 5: Memory stalling

Figure 5 shows that the processor stalled for the LDR instruction (instruction 40) to finish before executing instruction 44, which accessed the destination register of instruction 40.

Appendix

```

1  /* arm is the spotlight of the show and contains the bulk of the datapath and control
2  */
3
4  // clk - system clock
5  // rst - system reset
6  // Instr - incoming 32 bit instruction from imem, contains opcode, condition, addresses and
   or immediates
7  // ReadData - data read out of the dmem
8  // WriteData - data to be written to the dmem
9  // MemW - write enable to allowed WriteData to overwrite an existing dmem word
10 // PC - the current program count value, goes to imem to fetch instruciton
11 // ALUResult - result of the ALU operation, sent as address to the dmem
12
13 module arm (
14     input logic clk, rst,
15     input logic [31:0] Instr,
16     input logic [31:0] ReadData,
17     output logic [31:0] WriteData,
18     output logic [31:0] PC, ALUResult,
19     output logic MemWrite
20 );
21
22 // datapath buses and signals
23 logic [31:0] PCF, PCPrime, PCPlus4F, PCPlus8D; // pc signals
24 logic [3:0] RA1D, RA2D, RA1E, RA2E; // regfile input addresses
25 logic [31:0] RD1D, RD2D, RD1E, RD2E; // raw regfile outputs
26 logic [3:0] ALUFlags, FlagsD, FlagsE; // alu combinational flag outputs
27 logic [31:0] ExtImmD, ExtImmeE, SrcAE, SrcBE; // immediate and alu inputs
28 logic [31:0] ResultW; // computed or fetched value to be written
   into regfile or pc
29
30 // control signals
31 logic PCSrcD, PCSrcE, PCSrcM, PCSrcW, PCWrPendingF;
32 logic RegWriteD, RegWriteE, RegWriteM, RegWriteW;
33 logic MemtoRegD, MemtoRegE, MemtoRegM, MemtoRegW;
34 logic MemWriteD, MemWriteE, MemWriteM;
35 logic [1:0] ALUControlD, ALUControlE;
36 logic BranchD, BranchE;
37 logic ALUSrcD, ALUSrcE;
38 logic [1:0] ImmSrcD;
39 logic Match_1E_M, Match_2E_M;
40 logic Match_1E_W, Match_2E_W;
41 logic Match_12D_E;
42 logic BranchTakenE, StallF, StallD, FlushD, FlushE, ldrStallD, CondEx, CondExE;
43 logic [1:0] FlagWriteD, FlagWriteE, RegSrcD;
44 logic [1:0] ForwardAE, ForwardBE;
45 logic [3:0] CondeE, WA3E, WA3M, WA3W;
46 logic [31:0] ALUOutW, ALUOutM;
47 logic [31:0] InstrF, InstrD;
48 logic [31:0] ReadDataM, ReadDataW;
49 logic [31:0] WriteDataE, WriteDataM;
50 logic [31:0] ALUResultE;
51
52
53 /* The datapath consists of a PC as well as a series of muxes to make decisions about
54 which data words to pass forward and operate on. It is
55 ** noticeably missing the register file and alu, which you will fill in using the
56 modules made in lab 1. To correctly match up signals to the
57 ** ports of the register file and alu take some time to study and understand the logic
58 and flow of the datapath.
59 */
60 //-----
61 //                                     DATAPATH
62 //-----
63
64 // connect module inputs and outputs to datapath
65 assign InstrF = Instr;
66 assign ReadDataM = ReadData;
67 assign WriteData = WriteDataM;
68 assign MemWrite = MemWriteM;
69 assign PC = PCF;
70 assign ALUResult = ALUOutM;
71
72 assign PCPrime = BranchTakenE ? ALUResultE : (PCSrcW ? ResultW : PCPlus4F); // mux,
   use either default or newly computed value

```



```

70     assign PCPlus4F = PCF + 'd4;                                // default value to access next instruction
71     assign PCPlus8D = PCPlus4F;                                // value read when reading from reg[15]
72
73     // update the PC, at rst initialize to 0
74     always_ff @(posedge clk) begin
75         if (rst) PCF <= '0;
76         else if (!StallF) PCF <= PCPrime;
77         else PCF <= PCF;
78     end
79
80     // determine the register addresses based on control signals
81     // RegSrcD[0] is set if doing a branch instruction
82     // RefSrc[1] is set when doing memory instructions
83     assign RA1D = RegSrcD[0] ? 4'd15 : InstrD[19:16];
84     assign RA2D = RegSrcD[1] ? InstrD[15:12] : InstrD[3:0];
85
86     // Instantiates a register file to hold values.
87     reg_file u_reg_file (
88         .clk (!clk),
89         .wr_en (RegWritew),
90         .write_data (Resultw),
91         .write_addr (WA3W),
92         .read_addr1 (RA1D),
93         .read_addr2 (RA2D),
94         .read_data1 (RD1D),
95         .read_data2 (RD2D)
96     );
97
98     // two muxes, put together into an always_comb for clarity
99     // determines which set of instruction bits are used for the immediate
100    always_comb begin
101        if (ImmSrcD == 'b00) ExtImmD = {{24{InstrD[7]}}, InstrD[7:0]}; // 8
102    bit immediate - reg operations
103        else if (ImmSrcD == 'b01) ExtImmD = {20'b0, InstrD[11:0]}; // 12
104    bit immediate - mem operations
105        else ExtImmD = {{6{InstrD[23]}}, InstrD[23:0], 2'b00}; // 24
106    bit immediate - branch operation
107    end
108
109    // WriteData and SrcA are direct outputs of the register file, whereas SrcB is chosen
110    // between reg file output and the immediate
111    assign SrcBE = ALUSrcE ? ExtImme : WriteDataE; // determine alu operand to be
112    // either from reg file or from immediate
113    // Depending on forwarding control signal from hazard unit, choose appropriate ALU
114    // operand
115    always_comb begin
116        case (ForwardAE)
117            2'b00: SrcAE = (RA1E == 'd15) ? (BranchTakenE ? PCPlus8D : PCF) : RD1E; //
118        substitute the 15th regfile register for PC
119            2'b01: SrcAE = Resultw;
120            2'b10: SrcAE = ALUOutM;
121            default: SrcAE = RD1E;
122        endcase
123
124        case (ForwardBE)
125            2'b00: WriteDataE = (RA2E == 'd15) ? (BranchTakenE ? PCPlus8D : PCF) : RD2E; //
126        substitute the 15th regfile register for PC
127            2'b01: WriteDataE = Resultw;
128            2'b10: WriteDataE = ALUOutM;
129            default: WriteDataE = RD2E;
130        endcase
131    end
132
133    // Instantiates an alu module to do arithmetic operations.
134    alu u_alu (
135        .a (SrcAE),
136        .b (SrcBE),
137        .ALUControl (ALUControlE),
138        .Result (ALUResultE),
139        .ALUFlags (ALUFlags)
140    );
141
142    // determine the result to run back to PC or the register file based on whether we used
143    // a memory instruction
144    assign Resultw = MemtoRegW ? ReadDataW : ALUOutW; // determine whether final

```

writeback result is from dmemory or alu

```

137
138 // input signals for the hazard unit
139 assign Match_1E_M = (RA1E == WA3M);
140 assign Match_2E_M = (RA2E == WA3M);
141 assign Match_1E_W = (RA1E == WA3W);
142 assign Match_2E_W = (RA2E == WA3W);
143 assign Match_12D_E = ((RA1D == WA3E) + (RA2D == WA3E));
144 assign PCWrPendingF = (PCSrcD + PCSrcE + PCSrcM) & !BranchTakenE;
145 assign BranchTakenE = BranchE & CondExE;
146
147 // Instantiate a conditional unit to manage flags register and determine instruction
execution
148 cond_unit u_cond_unit (
149     .cond      (CondE),
150     .flags     (FlagsE),
151     .ALUFlags  (ALUFlags),
152     .flag_write (FlagWriteE),
153     .flags_out  (FlagsD),
154     .cond_ex   (CondExE)
155 );
156
157 // Instantiate a hazard unit to provide stalling, flushing, and forwarding control
signals
158 hazard_unit u_hazard_unit (
159     .Match_1E_M (Match_1E_M),
160     .Match_2E_M (Match_2E_M),
161     .Match_1E_W (Match_1E_W),
162     .Match_2E_W (Match_2E_W),
163     .Match_12D_E (Match_12D_E),
164     .RegWriteM   (RegWriteM),
165     .RegWriteW   (RegWriteW),
166     .MemtoRegE   (MemtoRegE),
167     .BranchTakenE (BranchTakenE),
168     .PCWrPendingF (PCWrPendingF),
169     .PCSrcW       (PCSrcW),
170     .ForwardAE    (ForwardAE),
171     .ForwardBE    (ForwardBE),
172     .StallF       (StallF),
173     .StallD       (StallD),
174     .FlushD       (FlushD),
175     .FlushE       (FlushE)
176 );
177
178 // Synchronously move signals along the datapath
179 always_ff @(posedge clk) begin
180     //Fetch to Decode
181     if (FlushD) InstrD <= 32'b0;
182     else if (!rst && !StallD) InstrD <= InstrF;
183
184     //Decode to Execute
185     if (!FlushE) begin
186         PCSrcE <= PCSrcD;
187         RegWriteE <= RegWriteD;
188         MemtoRegE <= MemtoRegD;
189         MemWriteE <= MemWriteD;
190         ALUControlE <= ALUControlD;
191         BranchE <= BranchD;
192         ALUSrcE <= ALUSrcD;
193         FlagWriteE <= FlagWriteD;
194         CondE <= InstrD[31:28];
195         FlagsE <= FlagsD;
196         RD1E <= RD1D;
197         RD2E <= RD2D;
198         RA1E <= RA1D;
199         RA2E <= RA2D;
200         WA3E <= InstrD[15:12];
201         ExtImmeE <= ExtImmeD;
202     end else begin
203         PCSrcE <= 0;
204         RegWriteE <= 0;
205         MemtoRegE <= 0;
206         MemWriteE <= 0;
207         ALUControlE <= 0;
208         BranchE <= 0;
209         ALUSrcE <= 0;

```

```

210     FlagWriteE <= 0;
211     CondE <= 4'b1111;
212     FlagsE <= 0;
213     RD1E <= 0;
214     RD2E <= 0;
215     WA3E <= 0;
216     ExtImmeE <= 0;
217 end
218
219 //Execute to Memory
220 if (!BranchTakenE) begin
221     PCSrcM <= PCSrcE & CondExE;
222     RegWriteM <= RegWriteE & CondExE;
223     MemtoRegM <= MemtoRegE;
224     MemWriteM <= MemWriteE & CondExE;
225     WriteDataM <= WriteDataE;
226     ALUOutM <= ALUResultE;
227     WA3M <= WA3E;
228 end
229
230 //Memory to writeback
231 ReadDataW <= ReadDataM;
232 ALUOutW <= ALUOutM;
233 WA3W <= WA3M;
234 PCSrcW <= PCSrcM;
235 RegWriteW <= RegWriteM;
236 MemtoRegW <= MemtoRegM;
237 end
238
239
240 /* The control consists of a large decoder, which evaluates the top bits of the
instruction and produces the control bits
** which become the select bits and write enables of the system. The write enables
(RegW, MemW and PCS) are
** especially important because they are representative of your processors current
state.
*/
//-----
//                                     CONTROL
//-----
247 always_comb begin
248     casez (InstrD[27:20])
249
250         // ADD (Imm or Reg)
251         8'b00?_0100_? : begin // note that we use wildcard "?" in bit 25. That bit
decides whether we use immediate or reg, but regardless we add
                PCSrcD = 0;
                MemtoRegD = 0;
                MemWriteD = 0;
                ALUSrcD = InstrD[25]; // may use immediate
                RegWriteD = 1;
                RegSrcD = 'b00;
                ImmSrcD = 'b00;
                ALUControlD = 'b00;
                FlagWriteD = {InstrD[20], InstrD[20]};
                BranchD = 0;
            end
262
263         // SUB/CMP (Imm or Reg)
264         8'b00?_0010_? : begin // note that we use wildcard "?" in bit 25. That bit
decides whether we use immediate or reg, but regardless we sub
                PCSrcD = 0;
                MemtoRegD = 0;
                MemWriteD = 0;
                ALUSrcD = InstrD[25]; // may use immediate
                RegWriteD = 1;
                RegSrcD = 'b00;
                ImmSrcD = 'b00;
                ALUControlD = 'b01;
                FlagWriteD = {InstrD[20], InstrD[20]};
                BranchD = 0;
            end
276
277         // AND
278         8'b000_0000_? : begin
                PCSrcD = 0;

```

```

281     MemtoRegD = 0;
282     MemWritED = 0;
283     ALUSrcD   = 0;
284     RegWritED = 1;
285     RegSrcD   = 'b00;
286     ImmSrcD   = 'b00;    // doesn't matter
287     ALUControlD = 'b10;
288     FlagWritED = {InstrD[20], 1'b0};
289     BranchD = 0;
290     //FlagWriteE = 00;
291 end
292
293 // ORR
294 8'b000_1100_? : begin
295     PCSrcD = 0;
296     MemtoRegD = 0;
297     MemWritED = 0;
298     ALUSrcD   = 0;
299     RegWritED = 1;
300     RegSrcD   = 'b00;
301     ImmSrcD   = 'b00;    // doesn't matter
302     ALUControlD = 'b11;
303     FlagWritED = {InstrD[20], 1'b0};
304     BranchD = 0;
305 end
306
307 // LDR
308 8'b010_1100_1 : begin
309     PCSrcD = 0;
310     MemtoRegD = 1;
311     MemWritED = 0;
312     ALUSrcD   = 1;
313     RegWritED = 1;
314     RegSrcD   = 'b10;    // msb doesn't matter
315     ImmSrcD   = 'b01;
316     ALUControlD = 'b00; // do an add
317     FlagWritED = 00;
318     BranchD = 0;
319 end
320
321 // STR
322 8'b010_1100_0 : begin
323     PCSrcD = 0;
324     MemtoRegD = 0; // doesn't matter
325     MemWritED = 1;
326     ALUSrcD   = 1;
327     RegWritED = 0;
328     RegSrcD   = 'b10;    // msb doesn't matter
329     ImmSrcD   = 'b01;
330     ALUControlD = 'b00; // do an add
331     FlagWritED = 00;
332     BranchD = 0;
333 end
334
335 // B
336 8'b1010_???? : begin
337     if(CondExE) begin
338         PCSrcD = 1;
339         MemtoRegD = 0;
340         MemWritED = 0;
341         ALUSrcD   = 1;
342         RegWritED = 0;
343         RegSrcD   = 'b01;
344         ImmSrcD   = 'b10;
345         ALUControlD = 'b00; // do an add
346         FlagWritED = 00;
347         BranchD = 1;
348     end else begin
349         PCSrcD = 0;
350         MemtoRegD = 0;
351         MemWritED = 0;
352         ALUSrcD   = 0;
353         RegWritED = 0;
354         RegSrcD   = 'b00;
355         ImmSrcD   = 'b00;    // doesn't matter
356         ALUControlD = 'b00;

```



```
357         FlagWriteD = 00;
358         BranchD = 0;
359     end
360 end
361
362 //      // CMP
363 //      8'b00?00101 : begin
364 //          PCS = 0;
365 //          MemtoRegD = 0;
366 //          MemW = 0;
367 //          ALUSrcD = Instr[25];
368 //          RegW = 1;
369 //          RegSrcD = 'b00;
370 //          ImmSrcD = 'b00;
371 //          ALUControlD = 'b01; // subtract
372 //          FlagWriteE = 11;
373 //      end
374
375 default: begin
376     PCSrcD = 0;
377     MemtoRegD = 0; // doesn't matter
378     MemWriteD = 0;
379     ALUSrcD = 0;
380     RegWriteD = 0;
381     RegSrcD = 'b00;
382     ImmSrcD = 'b00;
383     ALUControlD = 'b00; // do an add
384     FlagWriteD = 00;
385     BranchD = 0;
386 end
387 endcase
388 end
389
390
391 endmodule
```

```
1  //Aaron Hong (ahong02)
2  //Stephen Macris (smacris)
3  //5/3/23
4  //EE469 Lab3
5
6  //This module creates an asynchronous conditional unit that manages the flags register
7  //and determines conditional execution.
8
9  module cond_unit (cond, flags, ALUFlags, flag_write, flags_out, cond_ex);
10
11     input logic [3:0] cond, flags, ALUFlags;
12     input logic [1:0] flag_write;
13     output logic cond_ex;
14     output logic [3:0] flags_out;
15
16     always_comb begin
17         case (cond)
18             4'b0000: cond_ex = flags[2];
19             4'b0001: cond_ex = !flags[2];
20             4'b0010: cond_ex = flags[1];
21             4'b0011: cond_ex = !flags[1];
22             4'b0100: cond_ex = flags[3];
23             4'b0101: cond_ex = !flags[3];
24             4'b0110: cond_ex = flags[0];
25             4'b0111: cond_ex = !flags[0];
26             4'b1000: cond_ex = !flags[2] && flags[1];
27             4'b1001: cond_ex = flags[2] || !flags[1];
28             4'b1010: cond_ex = !(flags[3] ^ flags[0]);
29             4'b1011: cond_ex = flags[3] ^ flags[0];
30             4'b1100: cond_ex = !flags[2] && !(flags[3] ^ flags[0]);
31             4'b1101: cond_ex = flags[2] || (flags[3] ^ flags[0]);
32             4'b1110: cond_ex = 1;
33             default: cond_ex = 0;
34         endcase
35
36         case (flag_write)
37             2'b11: flags_out = ALUFlags;
38             2'b10: flags_out = {ALUFlags[3:2], 2'b00};
39             2'b01: flags_out = {2'b00, ALUFlags[1:0]};
40             2'b00: flags_out = 4'b0000;
41             default: flags_out = 4'b0000;
42         endcase
43     end
44
45 endmodule
46
47
```

```
1  //Aaron Hong (ahong02)
2  //Stephen Macris (smacris)
3  //5/3/23
4  //EE469 Lab3
5
6  //This module creates an asynchronous hazard unit that outputs stalling, flushing, and
   forwarding control signals.
7
8  module hazard_unit (
9      input logic Match_1E_M, Match_2E_M,
10     input logic Match_1E_W, Match_2E_W,
11     input logic Match_12D_E,
12     input logic RegWriteM, RegWriteW, MemtoRegE, BranchTakenE, PCWrPendingF, PCSrcW,
13     output logic [1:0] ForwardAE, ForwardBE,
14     output logic StallF, StallD, FlushD, FlushE
15 );
16
17     logic ldrStallD;
18
19     assign ldrStallD = Match_12D_E & MemtoRegE;
20
21     assign StallF = ldrStallD + PCWrPendingF;
22     assign FlushD = PCWrPendingF + PCSrcW + BranchTakenE;
23     assign FlushE = ldrStallD + BranchTakenE;
24     assign StallD = ldrStallD;
25
26     always_comb begin
27         if (Match_1E_M && RegWriteM) ForwardAE = 2'b10;
28         else if (Match_1E_W && RegWriteW) ForwardAE = 2'b01;
29         else ForwardAE = 2'b00;
30
31         if (Match_2E_M && RegWriteM) ForwardBE = 2'b10;
32         else if (Match_2E_W && RegWriteW) ForwardBE = 2'b01;
33         else ForwardBE = 2'b00;
34     end
35
36 endmodule
37
38
```