

```
1  //Aaron Hong (ahong02)
2  //Stephen Macris (smacris)
3  //3/29/23
4  //EE469 Lab1
5
6  //This module creates a basic arithmetic logic unit capable of addition, subtraction,
7  //ANDing, and ORing.
8
9  //Inputs: Two 32-bits a, b (inputs to be processed), one 2-bit ALUControl (controls which
10 //Outputs: One 32-bit Result (result of chosen operation), one 4-bit ALUFlags (flags thrown
11 //depending on the result).
12 module alu (a, b, ALUControl, Result, ALUFlags);
13     input logic [31:0] a, b;
14     input logic [1:0] ALUControl;
15     output logic [31:0] Result;
16     output logic [3:0] ALUFlags;
17     logic cout, x, diff_sign;
18     logic [31:0] sum, b_mod;
19
20     assign x = ~ALUControl[0] & ~ALUControl[1] & (a[31] == b[31]);
21     assign diff_sign = a[31] ^ sum[31];
22
23     //Instantiates a 32-bit full adder to do addition and subtraction operations.
24     fulladder32 FA(.A(a), .B(b_mod), .cin(ALUControl[0]), .sum(sum), .cout(cout));
25
26     //Determines what operation to perform depending on ALUControl.
27     always_comb begin
28         case (ALUControl[0])
29             1'b0: b_mod = b;
30             1'b1: b_mod = ~b;
31         endcase;
32
33         case (ALUControl)
34             2'b00: Result = sum;
35             2'b01: Result = sum;
36             2'b10: Result = a & b;
37             2'b11: Result = a | b;
38         endcase
39
40         ALUFlags[3] = Result[31];
41         ALUFlags[2] = (Result == 32'b0);
42         ALUFlags[1] = ~ALUControl[1] & cout;
43         ALUFlags[0] = x & diff_sign & ~ALUControl[1];
44     end
45 endmodule
```